 


EXPERIMENT-9

- Title: Sequential logic
- Objective: Implementation of sequential logic.
- Course Outcome: CO3
- Bloom's Level: Analysis
- Problem Statement: Write a verilog program to design, simulate and test circuits of following flipflops -
 - A) D Flipflop
 - B) S-R Flipflop
 - C) J-K Flipflop
 - D) T Flipflop.

A D Flipflop

- Theory: A D (or delay) flipflop is a sequential circuit used to delay the change of state of its output signal (Q) until the next rising or falling edge of a clock timing input signal occurs. Here, output remains constant unless changed by altering the state of D input followed by a clock signal.
- Logic Diagram:



□ Truth Table :

CLK	D	Q(t)	$\bar{Q}(t)$	REMARKS
L	X	Q(t-1)	$\bar{Q}(t-1)$	PREVIOUS STATE
H	L	L	H	RESET
H	H	H	L	SET

□ Design Code :

```

module d-ff(clk, d, q, qbar);
    input clk;
    input d;
    output reg q = 0;    output qbar;

    assign qbar = ~q;
    always @(posedge clk)
        begin
            q <= d;
        end
endmodule

```

□ Testbench Code :

```

module d-ff-tb();
    reg CLK;
    reg D;
    wire Q, QBAR;
    d-ff uut(.clk(CLK), .d(D), .q(Q), .qbar(QBAR));

    initial begin
        $dumpfile("dump.red"); $dumpvars(1);
    end
endmodule

```




```

CLK = 0 ;
D = 0 ; # 5 ;
D = 1 ; # 5 ;
D = 0 ; # 5 ;
D = 1 ; # 5 ;
$ finish ;
end
always #2 CLK = ~CLK ;
endmodule

```


□ Timing Diagram:

 

□ S-R Flip Flop

□ Theory: SR FF is a 1 bit memory bistable device having two inputs i.e. SET and RESET. The SET input 'S' set the device or produce the output '1' in 'Q' terminal whereas RESET input 'R' reset the device and produce output '0' in 'Q' terminal. If both 'S' and 'R' are active simultaneously then the S-R ff goes to a invalid state where $Q = \bar{Q}$ happens.

□ Logic Diagram:

 

□ Truth Table:

CLK	S	R	Q(t)	$\bar{Q}(t)$	REMARKS
L	X	X	Q(t-1)	$\bar{Q}(t-1)$	PREVIOUS STATE
H	L	L	Q(t-1)	$\bar{Q}(t-1)$	NO CHANGE
H	L	H	L	H	RESET
H	H	L	H	L	SET
H	H	H	-	-	INVALID

□ Design Code:

```


module sr_ff (sr, clk, q, qbar);
    input [1:0] sr;
    input clk;
    output reg q = 0; output qbar;
    assign qbar = ~q;
    always @ (posedge clk)
        begin
            case (sr)
                2'b00 : begin q <= q; end
                2'b01 : begin q <= 0; end
                2'b10 : begin q <= 1; end
                2'b11 : begin q <= 1'bX; end
            endcase
        end
endmodule

```


□ Testbench Code:

```
module sr_ff_tb();  
    reg [1:0] SR;  
    reg CLK;  
    wire Q, QBAR;  
    sr_ff uut (.sr(SR), .clk(CLK), .q(Q), .qbar(QBAR));  
    initial begin  
        $dumpfile("dump.vcd"); $dumpvars(1);  
        CLK = 0;  
        SR = 2'b00 ; #5;  
        SR = 2'b01 ; #5;  
        SR = 2'b10 ; #5;  
        SR = 2'b11 ; #5;  
        $finish;  
    end  
    always #2 CLK = ~CLK;  
endmodule
```


□ Timing Diagram:

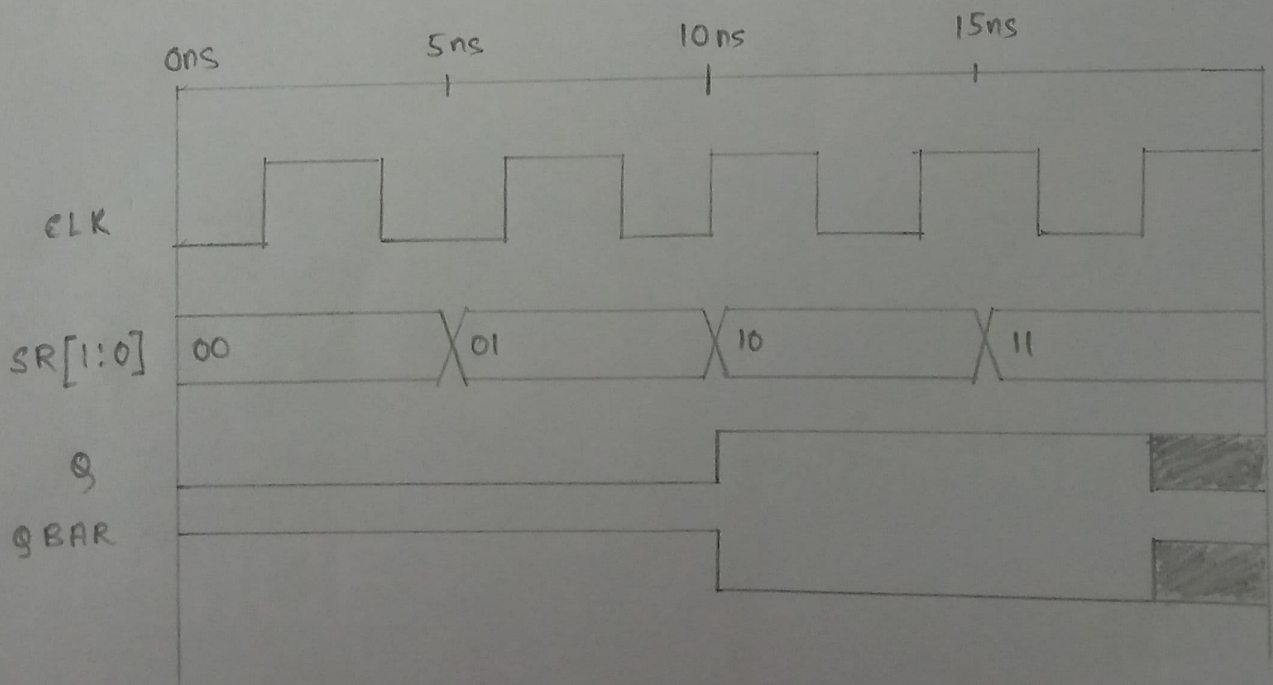

□ J-K Flipflop

□ Theory: JK flipflop is basically a gated SR flipflop with addition of clock circuit input. When both the inputs 'S' and 'R' are equal to logic '1', the invalid condition takes place. Thus to prevent this condition, a clock circuit is introduced. The J-K flipflop has four possible input combinations "logic 1", "logic 0", "No change" and "toggle". Here, cross-coupling of S-R flipflop is used to generate the 'Toggle' action.

□ Logic Diagram:

 

□ Truth Table:

CLK	J	K	$Q(t)$	$\bar{Q}(t)$	REMARKS
L	X	X	$Q(t-1)$	$\bar{Q}(t-1)$	PREVIOUS STATE
H	L	L	$Q(t-1)$	$\bar{Q}(t-1)$	NO CHANGE
H	L	H	L	H	RESET
H	H	L	H	L	SET
H	H	H	$\bar{Q}(t-1)$	$Q(t-1)$	TOGGLE


□ Design Code:

```
module jk-ff (jk, clk, q, qbar);  
    input [1:0] jk;  
    input clk;  
    output reg q = 0; output qbar;  
    assign qbar = ~q;  
    always @(posedge clk)  
        begin  
            case (jk)  
                2'b00 : begin q <= q; end  
                2'b01 : begin q <= 0; end  
                2'b10 : begin q <= 1; end  
                2'b11 : begin q <= ~q; end  
            endcase  
        end  
endmodule
```

□ Testbench Code:

```
module jk-ff-tb();  
    reg [1:0] JK; reg CLK;  
    wire Q, QBAR;  
    jk-ff uut (.jk(JK), .clk(CLK), .q(Q), .qbar(QBAR));  
    initial begin  
        $dumpfile("dump.vcd"); $dumpvars(1);  
        CLK = 0;  
        JK = 2'b00; #5;  
        JK = 2'b01; #5;  
        JK = 2'b10; #5;  
        JK = 2'b11; #5;  
        $finish;  
    end  
endmodule
```


□ Timing Diagram:

 

□ T Flipflop

□ Theory: T flipflop is also known as 'Toggle' Flipflop. Toggling means changing the next state output to complement of present state output. We can design T ff by making simple modifications to JK flipflop by connecting J and K inputs together and giving them with single input called 'T'.

□ Logic Diagram:

 

□ Truth Table

CLK	T	Q(t)	$\bar{Q}(t)$	REMARKS
L	X	Q(t-1)	$\bar{Q}(t-1)$	NO CHANGE
H	L	Q(t-1)	$\bar{Q}(t-1)$	NO CHANGE
H	H	$\bar{Q}(t-1)$	Q(t-1)	TOGGLE

□ Design Code:

```

module t-ff (clk, t, q, qbar);
    input clk, t;
    output reg q = 0;
    output qbar;
    assign qbar = ~q;
    always @ (posedge clk)
        begin
            if (t == 1) begin
                q <= ~q; end
        end
    end
endmodule

```

□ Testbench Code :

```

module t-ff-tb();
    reg CLK;
    reg T;
    wire Q, QBAR;
    t-ff uut (.clk(CLK), .t(T), .q(Q), .qbar(QBAR));
    initial begin
        $dumpfile("dump.rcd");
        $dumpvars(1);
    end
endmodule

```

```


CLK=0 ;
T=0 ; # 5 ;
T=1 ; # 5 ;
T=1 ; # 5 ;
T=1 ; # 5 ;
T=1 ; # 5 ;

```

end

endmodule

□ Timing Diagram:

 


□ Discussion: In this experiment, we have implemented various sequential circuits like flipflops. We have learned about 'always @' keyword and many other keywords in verilog.

□ Justification of CO: In this experiment, we have implemented various sequential circuits which fulfills the conditions of CO3. Hence, CO3 is justified.



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

D FLIPFLOP

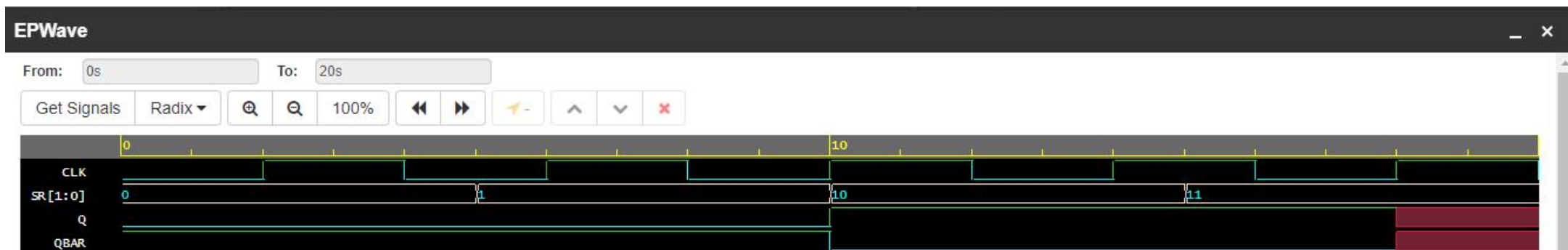


Note: To revert to EPWave opening in a new browser window, set that option on your user page.

SR FLIPFLOP



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

JK FLIPFLOP

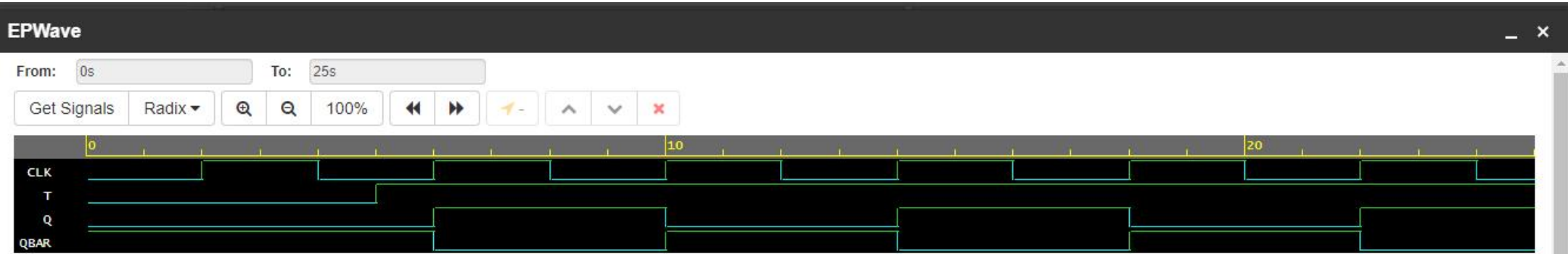

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

T FLIPFLOP