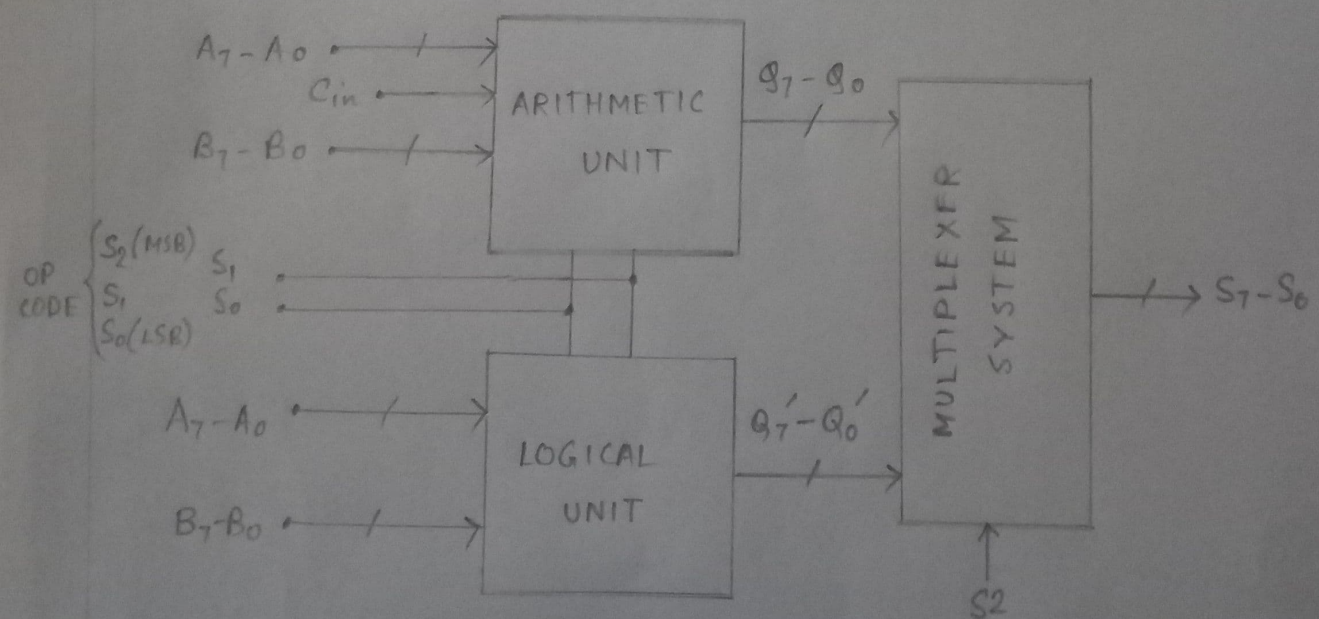


### EXPERIMENT-13

- Title: Arithmetic and Logical Unit (ALU)
- Objective: Implementation of ALU
- Course Outcome: CO6
- Bloom's Level: Comprehension
- Problem Statement: Write a verilog program to implement an 8 bit ALU which will perform following function table.
- Theory: Arithmetic logic unit (ALU) is an important part of microprocessor. In digital processors logical and arithmetic operation executes using ALU. In this experiment we have implemented a 8 bit ALU circuit using MUX's and parallel adders. Based on selection lines of every Mux, a specific arithmetical or logical operation is selected and executed.
- Logic Diagram:





## Function Table:

OPCODE	OPERATION	REMARKS
L L L	$A - B$	without carry
L L H	$A + B$	w/o carry
L H L	$A + B + C_{in}$	with carry
L H H	$A - B - C_{in}$	with carry
H L L	$A \wedge B$	XOR operation
H L H	$\sim B$	NOT operation
H H L	$A   B$	OR operation
H H H	$A \& B$	AND operation

(A & B are 2  
8 bit no.)

OPCODE  
 $S_2 \ S_1 \ S_0$   
 $\downarrow \quad \downarrow$   
 (MSB) (LSB)

## Design Code :

```
module mux_4to1(input a0, input a1, input a2, input a3,
               input [1:0] s, output y);
```

```
    assign y = s[1] ? (s[0] ? a[3] : a[2]) : (s[0] ? a[1] : a[0]);
```

```
endmodule
```

```
module mux_2to1(input a, input b, input s, output y);
```

```
    assign y = s ? b : a;
```

```
endmodule
```

```
module full_adder(input a, b, c, output s, cout);
```

```
    assign s = a ^ b ^ c;
```

```
    assign cout = (a & b) | (c & (a ^ b));
```

```
endmodule
```

```
module adder_subtractor(input [7:0] a, input [7:0] b, input
                      c0, output [7:0] s, output cout);
```

```
    wire c1, c2, c3, c4, c5, c6, c7;
```

```
    full_adder f1(a[0], b[0], c[0], s[0], c1);
```

```
    full_adder f2(a[1], b[1], c[1], s[1], c2);
```

```
    full_adder f3(a[2], b[2], c[2], s[2], c3);
```

```
    full_adder f4(a[3], b[3], c[3], s[3], c4);
```

```
    full_adder f5(a[4], b[4], c[4], s[4], c5);
```



```

full-adder f6 (a[5], b[5], c5, s[5], c6);
full-adder f7 (a[6], b[6], c6, s[6], c7);
full-adder f8 (a[7], b[7], c7, s[7], cout);

```

endmodule

```

module arithmetic (input [7:0] a, input [7:0] b, input cin,
input [1:0] sel, output [7:0] out0,
output cout);

```

```

wire [7:0] y0;

```

```

wire carry;

```

```

mux_4to1 uut1 (~b[0], b[0], b[0], ~b[0], sel[1:0], y0[0]);
mux_4to1 uut2 (~b[1], b[1], b[1], ~b[1], sel[1:0], y0[1]);
mux_4to1 uut3 (~b[2], b[2], b[2], ~b[2], sel[1:0], y0[2]);
mux_4to1 uut4 (~b[3], b[3], b[3], ~b[3], sel[1:0], y0[3]);
mux_4to1 uut5 (~b[4], b[4], b[4], ~b[4], sel[1:0], y0[4]);
mux_4to1 uut6 (~b[5], b[5], b[5], ~b[5], sel[1:0], y0[5]);
mux_4to1 uut7 (~b[6], b[6], b[6], ~b[6], sel[1:0], y0[6]);
mux_4to1 uut8 (~b[7], b[7], b[7], ~b[7], sel[1:0], y0[7]);

```

```

assign carry = (sel[1] ^ sel[0]) ? cin : (~cin);

```

```

adder-subtractor xxl(a[7:0], y0[7:0], carry, out0[7:0], cout);

```

endmodule

```

module logical (input [7:0] a, input [7:0] b, input [2:0] sel,
output [7:0] out);

```

```

mux_4to1 ut1 ((a[0] ^ b[0]), (~b[0]), (a[0] | b[0]), (a[0] & b[0]),
sel[1:0], out1[0]);
mux_4to1 ut2 ((a[1] ^ b[1]), (~b[1]), (a[1] | b[1]), (a[1] & b[1]),
sel[1:0], out1[1]);
mux_4to1 ut3 ((a[2] ^ b[2]), (~b[2]), (a[2] | b[2]), (a[2] & b[2]),
sel[1:0], out1[2]);
mux_4to1 ut4 ((a[3] ^ b[3]), (~b[3]), (a[3] | b[3]), (a[3] & b[3]),
sel[1:0], out1[3]);
mux_4to1 ut5 ((a[4] ^ b[4]), (~b[4]), (a[4] | b[4]), (a[4] & b[4]),
sel[1:0], out1[4]);
mux_4to1 ut6 ((a[5] ^ b[5]), (~b[5]), (a[5] | b[5]), (a[5] & b[5]),
sel[1:0], out1[5]);

```



```

mux-4to1 vut7((a[6] ^ b[6]), (~b[6]), (a[6] | b[6]), (a[6] & b[6]),
               sel[1:0], out1[6]);
mux-4to1 vut8((a[7] ^ b[7]), (~b[7]), (a[7] | b[7]), (a[7] & b[7]),
               sel[1:0], out1[7]);

```

endmodule

```

module alu(input [7:0] a, input [7:0] b, input cin, input [2:0] sel,
           output [7:0] out, output [7:0] out1, output
           [7:0] out0, output cout);

```

```

    arithmetic f1(a[7:0], b[7:0], cin, sel[1:0], out0[7:0], cout);

```

```

    logical f2(a[7:0], b[7:0], sel[1:0], out1[7:0]);

```

```

    mux-2to1 vut1(out0[0], out1[0], sel[2], out[0]);

```

```

    mux-2to1 vut2(out0[1], out1[1], sel[2], out[1]);

```

```

    mux-2to1 vut3(out0[2], out1[2], sel[2], out[2]);

```

```

    mux-2to1 vut4(out0[3], out1[3], sel[2], out[3]);

```

```

    mux-2to1 vut5(out0[4], out1[4], sel[2], out[4]);

```

```

    mux-2to1 vut6(out0[5], out1[5], sel[2], out[5]);

```

```

    mux-2to1 vut7(out0[6], out1[6], sel[2], out[6]);

```

```

    mux-2to1 vut8(out0[7], out1[7], sel[2], out[7]);

```

endmodule

□ Testbench Code:

```

module alu_tb1();

```

```

    reg [7:0] A;

```

```

    reg [7:0] B;

```

```

    reg cin;

```

```

    reg [2:0] SEL;

```

```

    wire [7:0] OUT;

```

```

    wire cout;

```

```

    alu uut(.a(A), .b(B), .cin(cin), .sel(SEL), .out(OUT), .cout(cout));

```

```

    initial begin

```

```

        $dumpfile("dump.red"); $dumpvars(1);

```

```

        A = 8'b11110000;

```

```

        B = 8'b00001111;

```

```

        cin = 0;

```

```

        SEL = 3'b000; #5;

```




```

SEL = 3'b 001 ; #5 ;
CIN = 1 ;
SEL = 3'b 010 ; #5 ;
SEL = 3'b 011 ; #5 ;
CIN = 0 ;
SEL = 3'b 100 ; #5 ;
SEL = 3'b 101 ; #5 ;
SEL = 3'b 110 ; #5 ;
SEL = 3'b 111 ; #5 ;

```

end  
endmodule

### □ Timing Diagram :

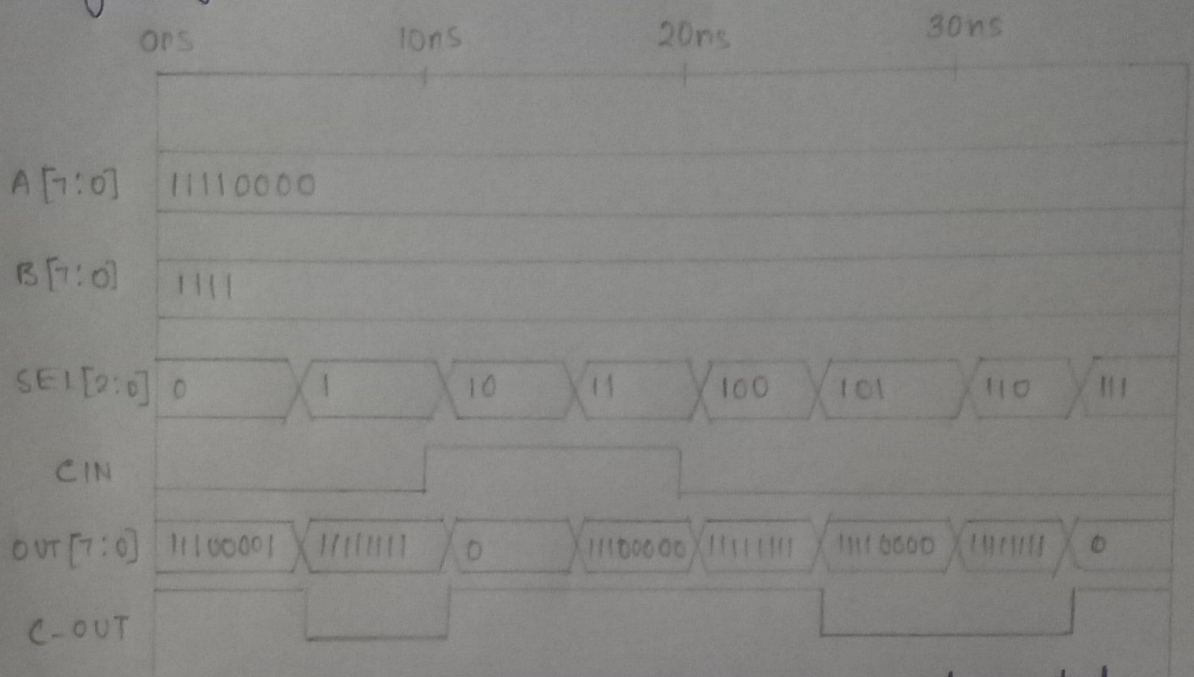

□ Discussion: In this experiment, we have implemented a 8bit ALU circuit using 4x1 and 2x1 MUX and a parallel adder-subtractor module. We came to know that this ALU works as a processing unit in computer system. We have learned various HDL terms also.

□ Justification of CO: In this experiment, we have designed an ALU circuit which is one of the most important processing element in a computer system. We made this circuit using verilog environment, which fulfills the conditions. Hence, COG is justified.

# EPWave


From: 0s To: 40s

Get Signals

Radix ▾



100%

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

ALU